

### 1. Effects of garbage in quantum circuits

The CNOT gate performs the mapping  $(i, j) \rightarrow (i, i + j \bmod 2)$  from an input on two bits  $(i, j \in \{0, 1\})$  to an output on two bits. It is interesting to note (though not relevant to the problem) that this mapping is not of the form  $(z, 0) \rightarrow (z, f(z))$  as considered last week, since the function  $f(i, j) = i + j \bmod 2$  does not require the whole input to be present in the output for reversibility.

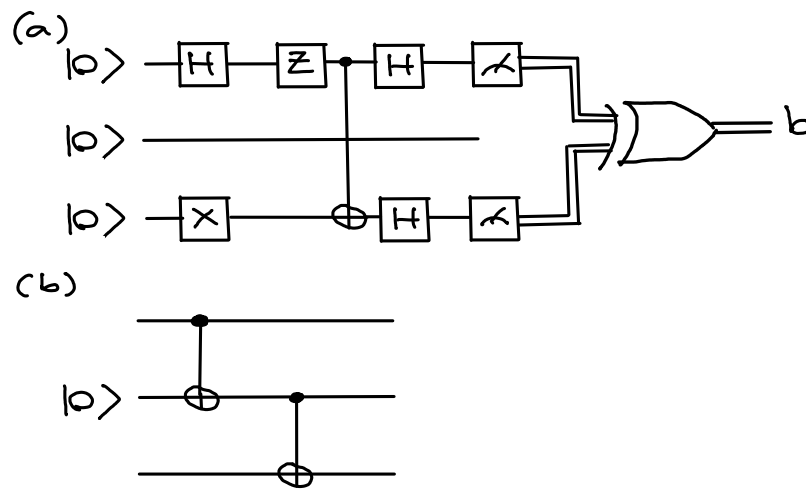


Figure 1: Circuits!

- Consider the circuit in Fig. 1 (a). This is composed of both a quantum part, and an irreversible classical part. Determine the value of the output bit  $b$ .
- Consider the circuit in Fig. 1 (b). Show that this effectively acts as a CNOT between the first and third qubits, but with the additional effect of producing a garbage output on the second.
- Replace the CNOT in Fig. 1 (a) with the element in Fig. 1 (b). Show that this changes the behaviour of the output bit  $b$ .
- Use uncomputation to ‘correct’ Fig. 1 (b) by removing the garbage.